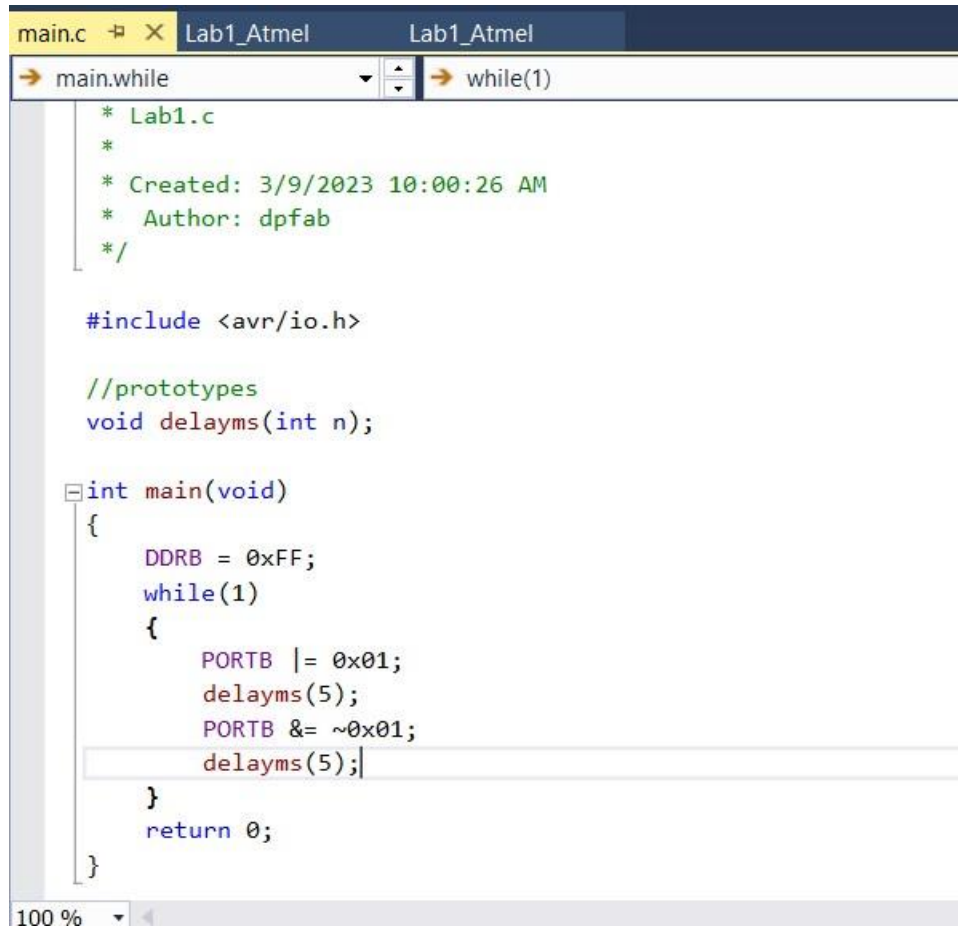


The goal of lab 1 was to begin the operation of testing the PCB to prove it as being functional. Measurements of the output of the 5-volt Regulator show were taken to prove that the power conditioning circuit was built and implemented properly, as well as shown to conditioning much higher voltages than should be needed (Figures 2-6). An LED was blinked through the use of PB0 on the microcontroller to prove that the ISP interface and microcontroller were both fully functional.

Issues were faced that impeded the completion of the lab. The first iteration of testing the power circuit showed that no power was reaching the board from the input. It was concluded that the issue stemmed from the regulator portion of the circuit. It was presumed that the regulator itself was the problem, but it is also possible that an internal connection was severed or had never existed in the first place. To remedy this, a second regulator was acquired and subsequently installed. During this process, the small pads the regulator is meant to be installed in were damaged. This led the regulator to being attached off the board and connected via soldered wires to capacitors attached to its input and output. Power was restored and successfully regulated after this. The Atmel Studio software was not allowing the code to be uploaded without restarting the software every single use. This is believed to be an issue with the software and did not impede completion of the exercise once the overall issues had been remedied, allowing for the blinking of the LED and proof that the ISP interfacing was successful.

To summarize, despite issues with the board, ISP IDE and general software, the 5-volt regulator successfully works, conditioning the input power and providing steady DC voltage sufficient for the microcontroller to operate. The ISP interfacing was also successfully demonstrated and allowed software to be installed on the controller to blink an LED.

# Appendix



The image shows a screenshot of an IDE window titled 'Lab1\_Atmel'. The editor displays C code for a program to blink an LED. The code includes a comment block with creation and author information, an include statement for <avr/io.h>, a prototype for delayms, and a main function. The main function sets DDRB to 0xFF and enters a while(1) loop. Inside the loop, it sets PORTB bit 0, calls delayms(5), toggles PORTB bit 0, and calls delayms(5) again. The code is formatted with syntax highlighting: comments in green, preprocessor directives in blue, and function calls in red. The IDE interface includes a tab bar at the top with 'main.c' and 'Lab1\_Atmel', a breadcrumb trail 'main.c > main.while > while(1)', and a status bar at the bottom showing '100 %'.

```
* Lab1.c
*
* Created: 3/9/2023 10:00:26 AM
* Author: dpfab
*/

#include <avr/io.h>

//prototypes
void delayms(int n);

int main(void)
{
    DDRB = 0xFF;
    while(1)
    {
        PORTB |= 0x01;
        delayms(5);
        PORTB &= ~0x01;
        delayms(5);
    }
    return 0;
}
```

Figure 1: Code used to blink LED

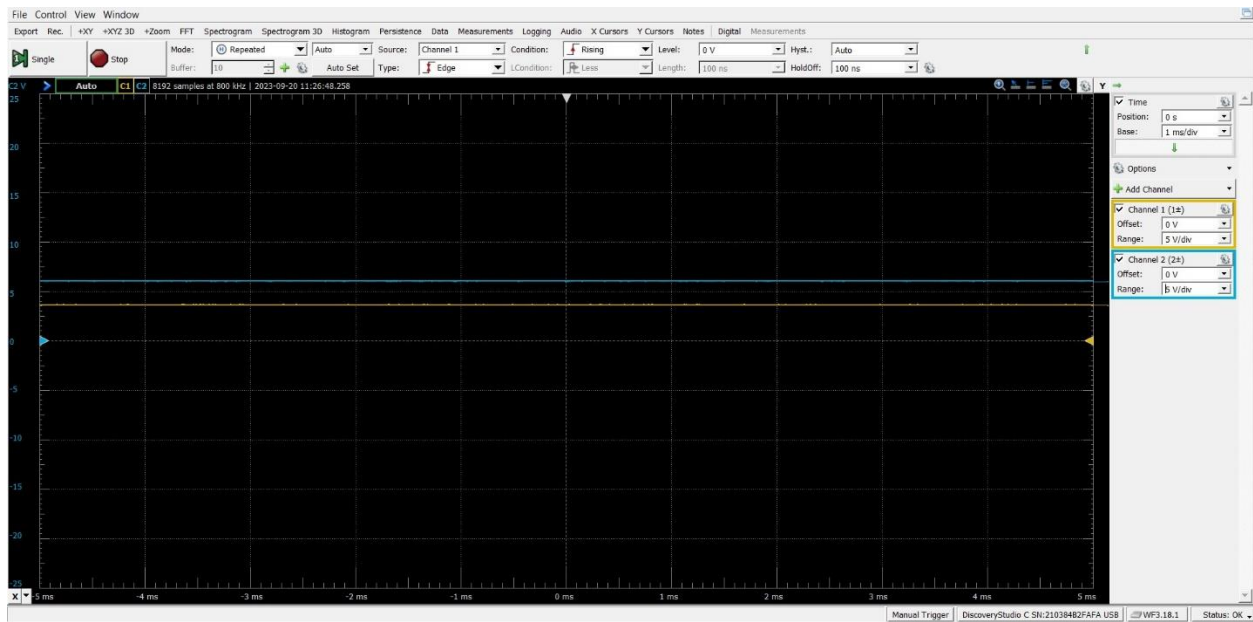


Figure 2: Input (blue) to voltage regulator of 6V and output (yellow) of under 5V

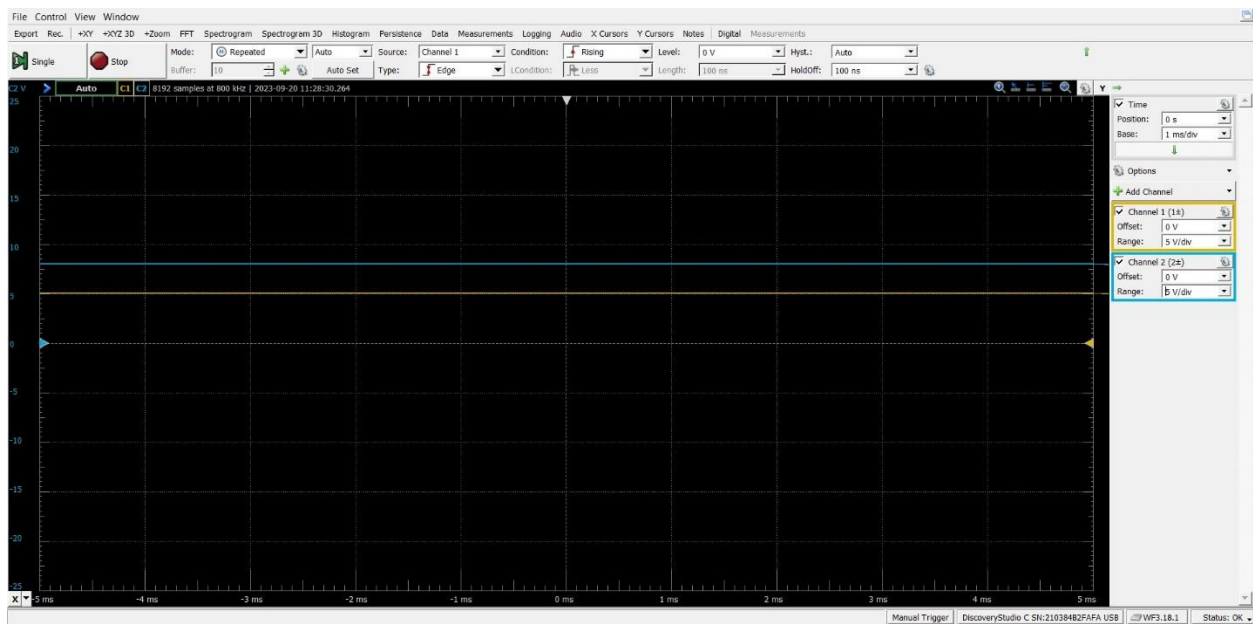


Figure 3: Input of 8V, resulting in just under 5V

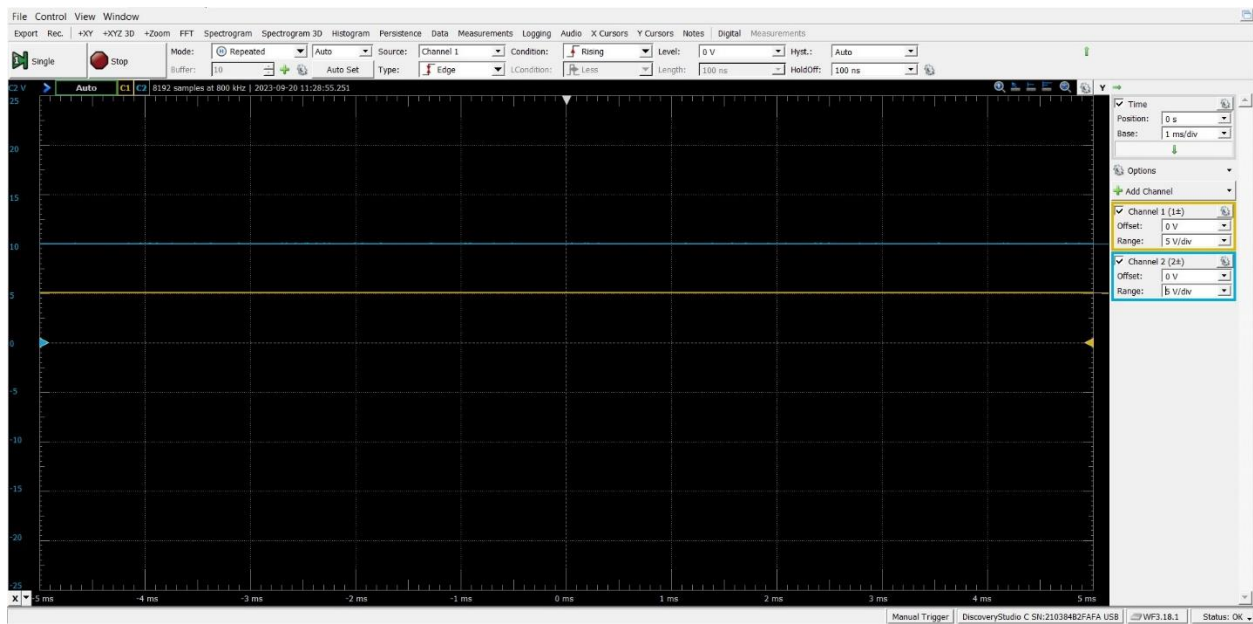


Figure 4: Input of 10V resulting in 5V

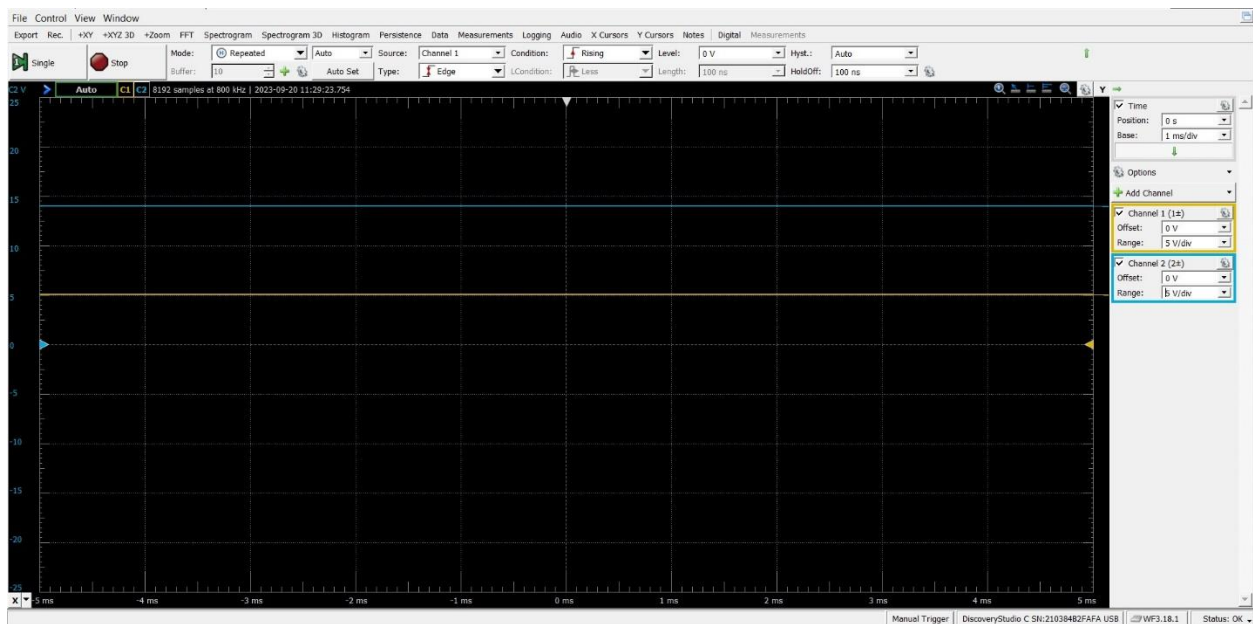


Figure 5: Input of 14V still results in 5V

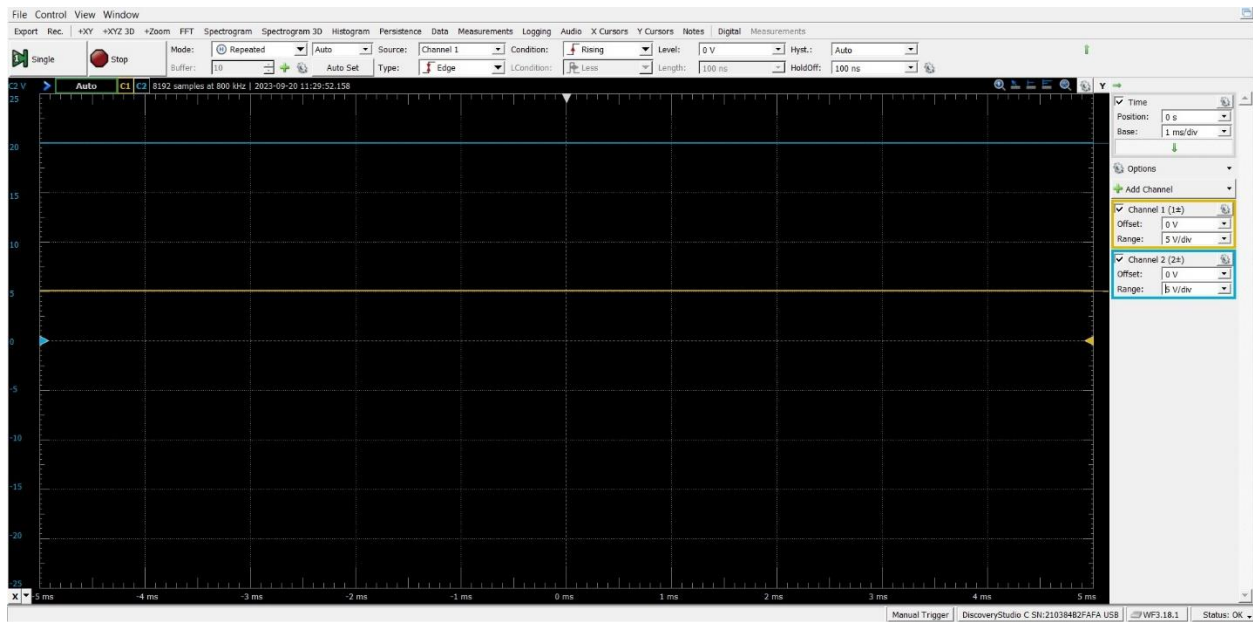


Figure 6: Input of 20V results in 5V

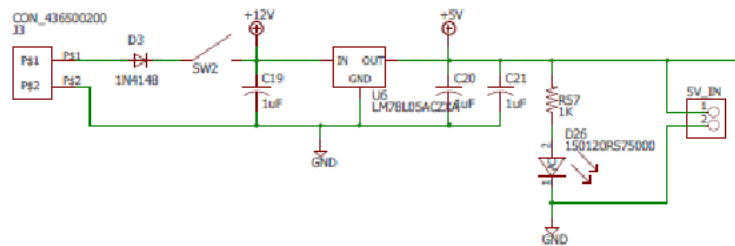


Figure 1  
Power Conditioning Circuit

Figure 7: Power Conditioning Circuit Schematic